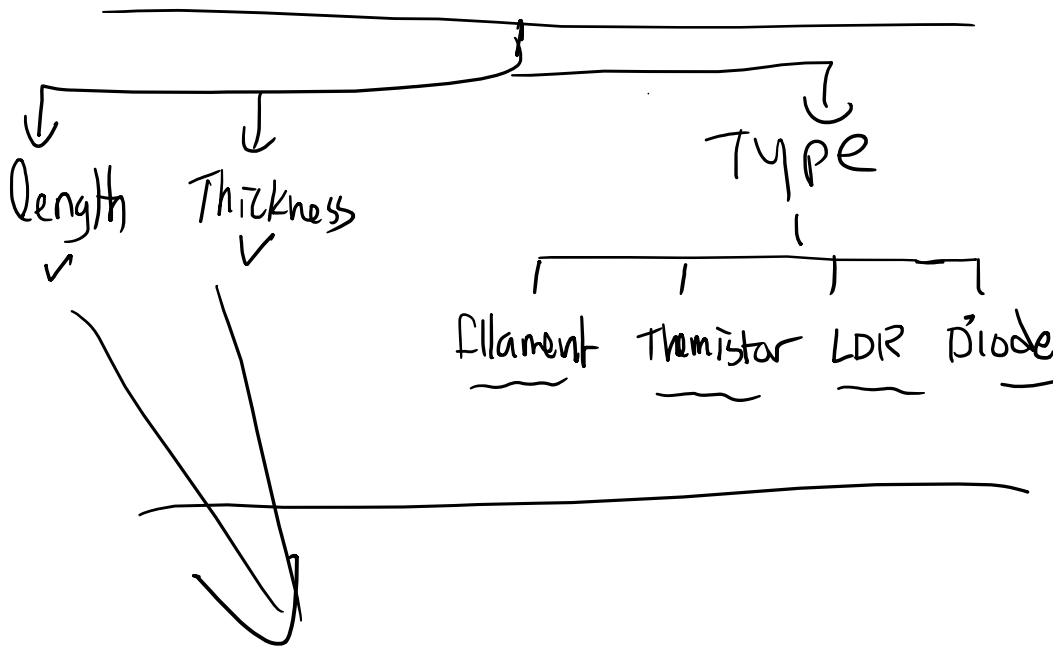


Some Resistors are not constant.



$$R \propto l$$

A resistor has $100\ \Omega$ of resistance.
 Its length is 20 cm . Calculate
 its resistance at a length of 60 cm .



$$R \propto l \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2}$$

$$= \frac{100}{R_2} = \frac{20}{60}$$

$$R_2 = \frac{100 \times 60}{20} = 300\ \Omega$$

$$R \propto \frac{1}{CSA}$$

cross-section
Area

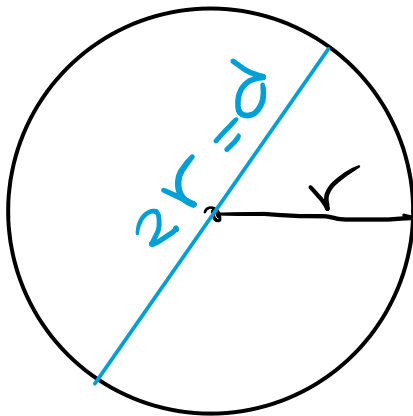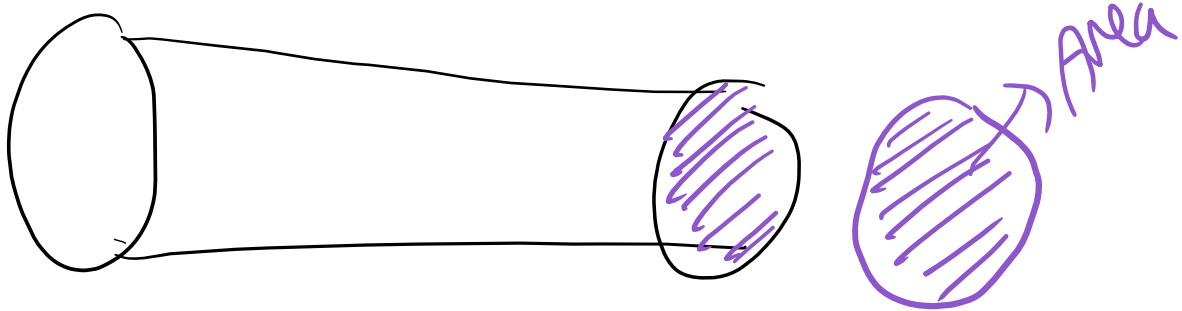


$$A = \pi r^2$$

$$r = \frac{\text{diameter}}{2}$$

$$\Rightarrow A = \pi \frac{d^2}{4}$$
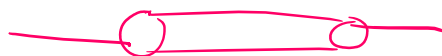
$$\left(\frac{d}{2}\right)^2 = \frac{d^2}{4}$$



A resistor of $100\ \Omega$ & CSA 2 cm^2
calculate its resistance if its
thickness becomes 0.5 cm^2

$$R_1 \propto \frac{1}{A_1}$$

$$\frac{R_1}{R_2} = \frac{A_2}{A_1}$$

$$\frac{100}{R_2} = \frac{0.5}{2}$$

$$R_2 = \frac{100 \times 2}{0.5} = 400\ \Omega$$

A wire of length 3cm & CSA of 4 cm² has a resistance of 100 Ω, another wire of the same material has a length of 5cm & CSA of 6 cm².
calculate its Resistance.

$$R \propto l \quad R \propto \frac{1}{A}$$

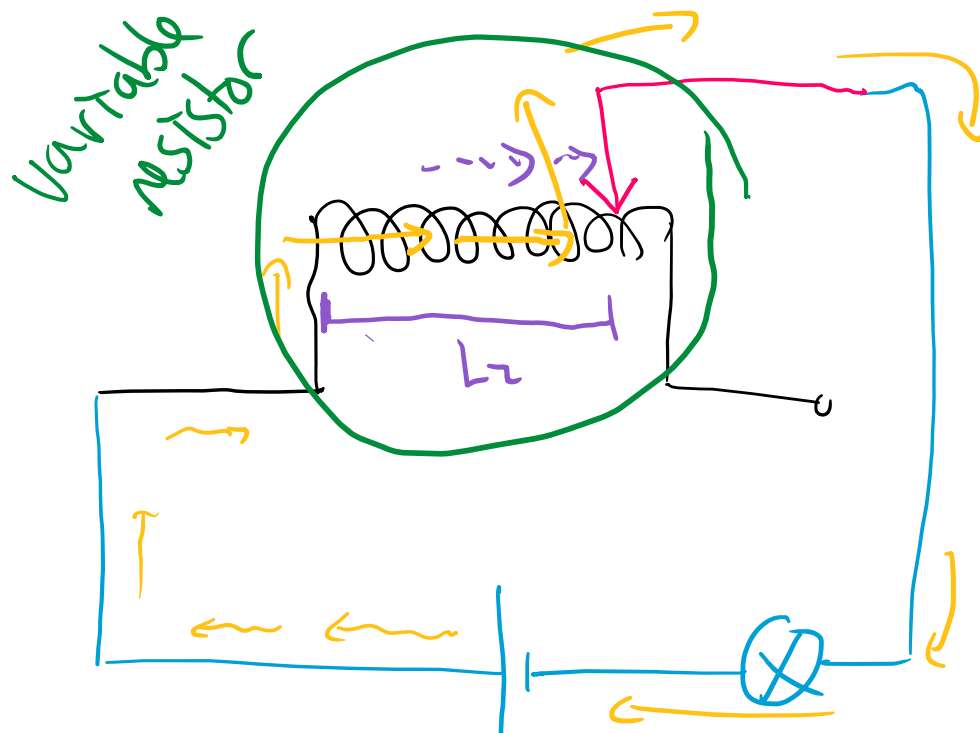
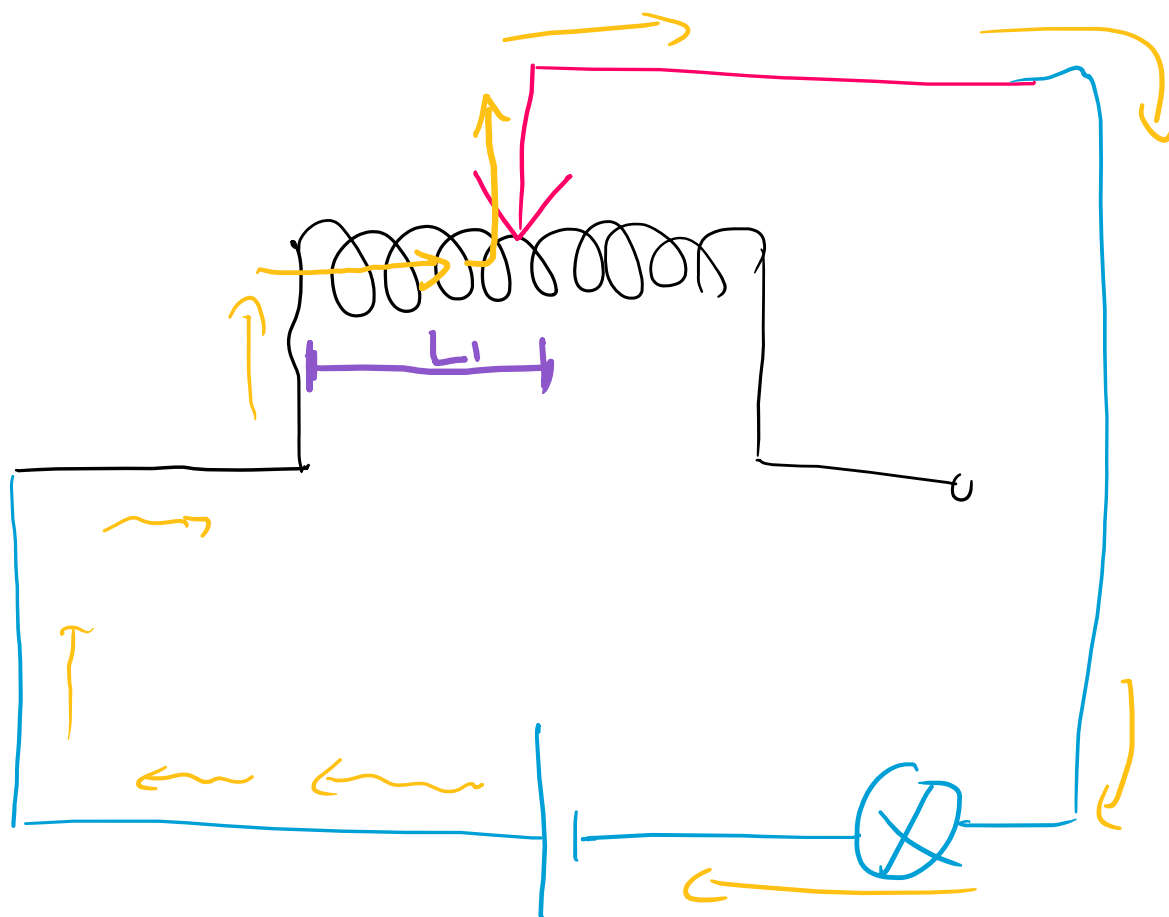

$$R \propto \frac{l}{A}$$

if I compare


$$\boxed{\frac{R_1}{R_2} = \frac{l_1 A_2}{l_2 A_1}}$$

$$\frac{100}{R_2} = \frac{4 \times 6}{5 \times 4}$$

$$R_2 = \frac{100 \times 5 \times 4}{4 \times 6} = 83.3 \Omega$$



$$\frac{R_1}{R_2} = \frac{L_1}{L_2}$$

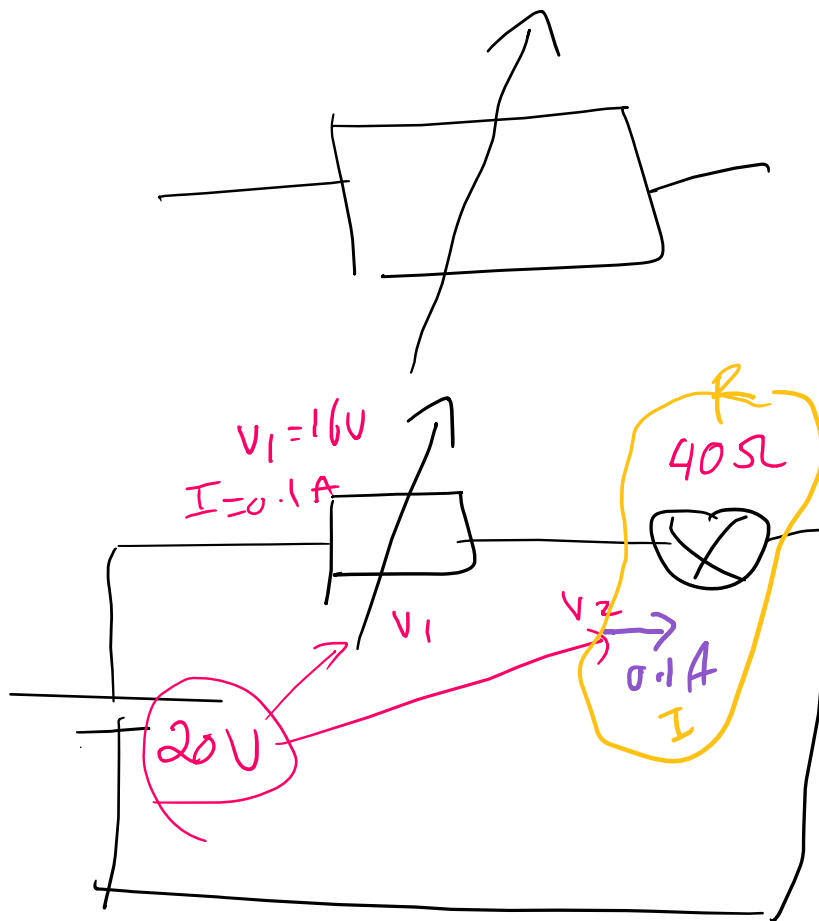

variable
Resistor.

$$V = IR$$

$$\frac{R_1}{R_2} = \frac{L_1 A_2}{L_2 A_1}$$

the lamp needs 0.1 Ampere to work properly. calculate the Resistance of the variable resistor

$$Emf = V_1 + V_2$$

$$\downarrow \quad \downarrow$$

$$20V = 16 + 4$$

$$V_2 = I_2 R_2$$


$$V_2 = 0.1 \times 40$$

$$= 4V$$

$$V_1 = I_1 R_1$$

$$R_1 = \frac{V_1}{I_1} = \frac{16}{0.1} = 160\Omega$$

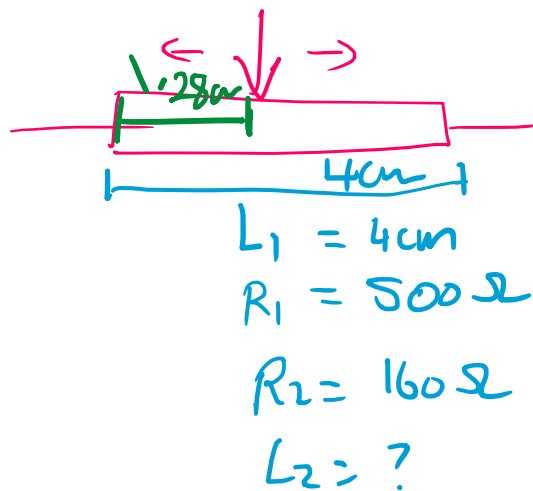If the total length of the variable resistor is 4cm, and its maximum resistance is 500Ω , calculate the length to adjust its resistance to 160Ω .



$$\frac{R_1}{R_2} = \frac{L_1}{L_2}$$

$$R_1 L_2 = R_2 L_1$$

$$L_2 = \frac{R_2 L_1}{R_1} = \frac{160 \times 4}{500} = 1.28\text{cm}$$

5 types of Resistors

1- Regular	2- Filament	3- Thermistor	4- LDR light dependent	5- Diode direction
Heat $\uparrow$ $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$	Heat $\uparrow$ $R \uparrow$ $V \uparrow$ $I \downarrow$	Heat $\uparrow$ $R \downarrow$ $V \downarrow$ $I \uparrow$	Light $\uparrow$ $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$	direction $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$
Light $\uparrow$ $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$	Light $\uparrow$ $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$	Light $\uparrow$ $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$	Light $\uparrow$ $R \downarrow$ $V \downarrow$ $I \uparrow$	direction $R \rightarrow \text{const}$ $V \rightarrow \text{const}$ $I \rightarrow \text{const}$
direction $\rightarrow$ $R \text{ const}$ $V \text{ const}$ $I \text{ const}$	$R \text{ const}$ $V \text{ const}$ $I \text{ const}$	$R \text{ const}$ $V \text{ const}$ $I \text{ const}$	$R \text{ const}$ $V \text{ const}$ $I \text{ const}$	direction 1 $R \downarrow \downarrow \downarrow$ almost zero $V \downarrow \downarrow \downarrow$ $I \uparrow \uparrow \uparrow$ direction 2 $R \uparrow \uparrow \uparrow$ $V \uparrow \uparrow \uparrow$ $I \text{ almost } 0$
		