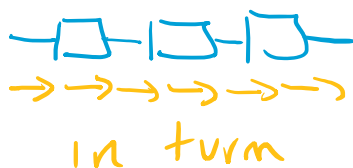


SeriesEmf ---|---|---

$$Emf = emf_1 + emf_2 + emf_3$$

$$V = V_1 + V_2 + V_3$$





$$V = V_1 + V_2 + V_3$$

current

$$I = I_1 = I_2 = I_3$$


resistance

$$R = R_1 + R_2 + R_3$$

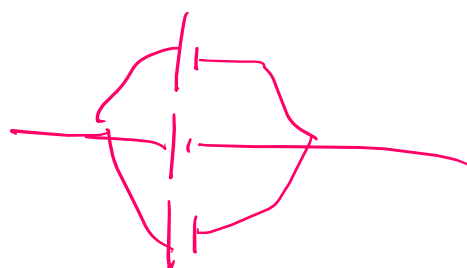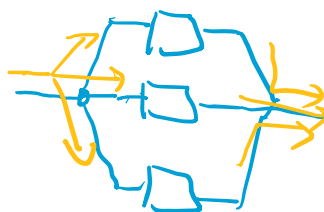Parallel

$$Emf = Emf_1 = Emf_2 = Emf_3$$

$$V = V_1 = V_2 = V_3$$

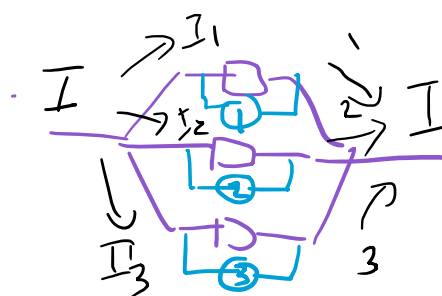


$$V = V_1 = V_2 = V_3$$

$$I = I_1 + I_2 + I_3$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


special case: only 2 R's

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

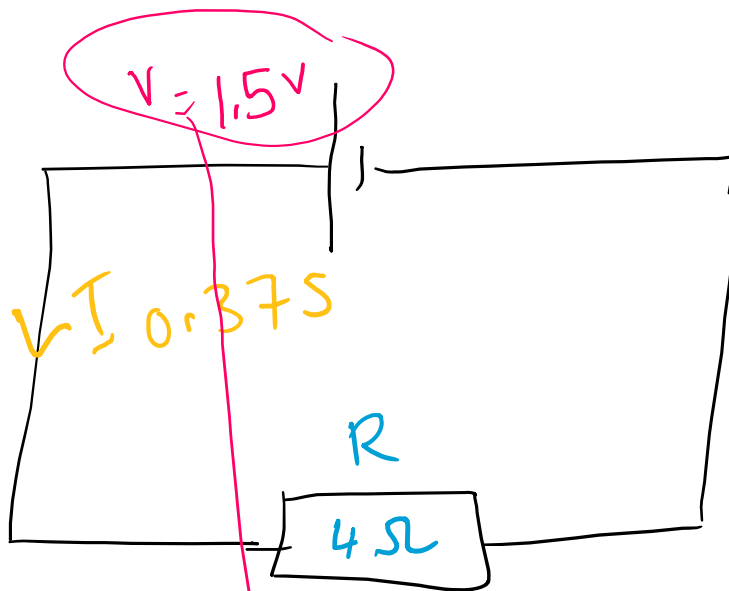


Ohm's Law

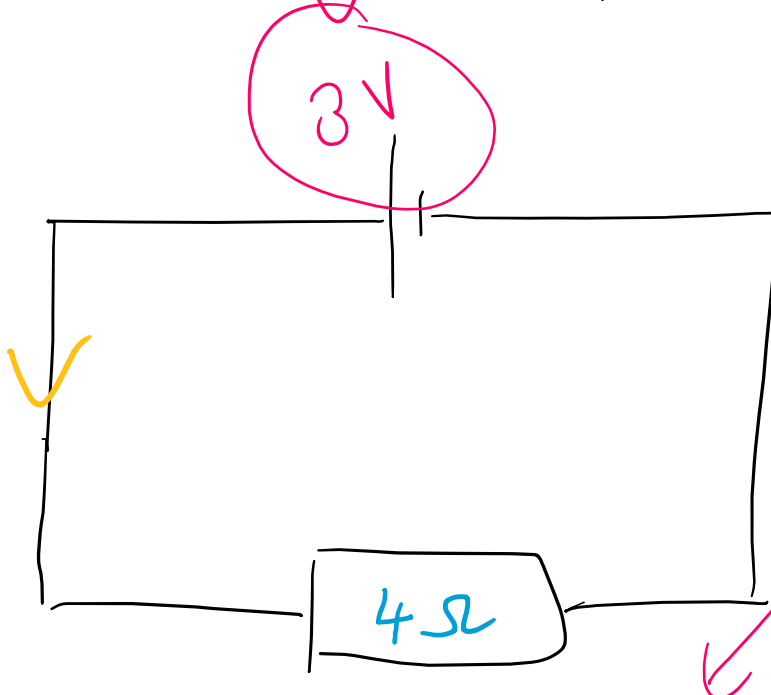
$$V = IR \quad I = \frac{V}{R} = \frac{1.5}{4} = 0.375\text{A}$$


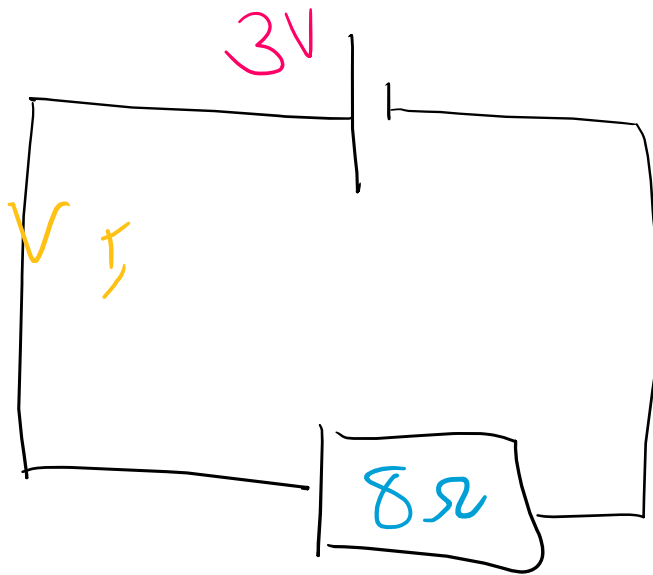
$$I = \frac{V}{R} = \frac{3}{4} = 0.75\text{A}$$



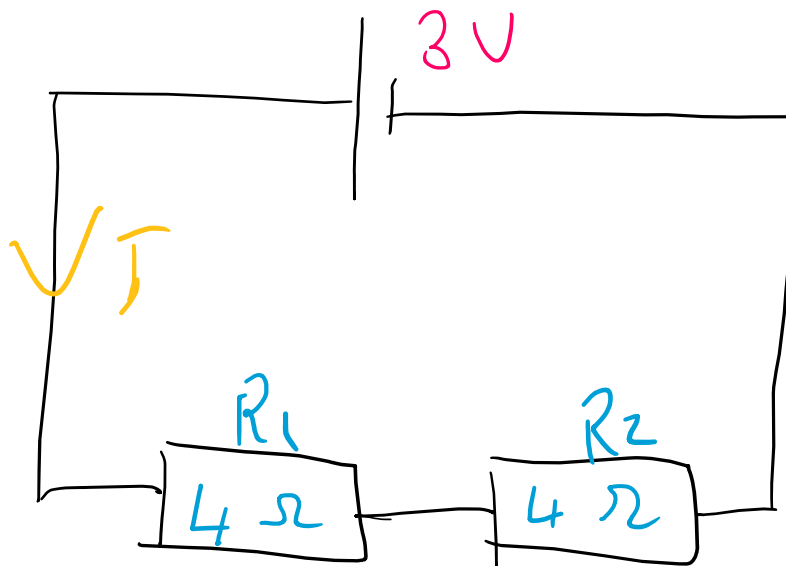
$$I = \frac{V}{R} = \frac{3}{8} = \boxed{0.375 \text{ A}}$$



$$I = \frac{V}{R}$$

$$R = R_1 + R_2 = 4 + 4 = 8\Omega$$
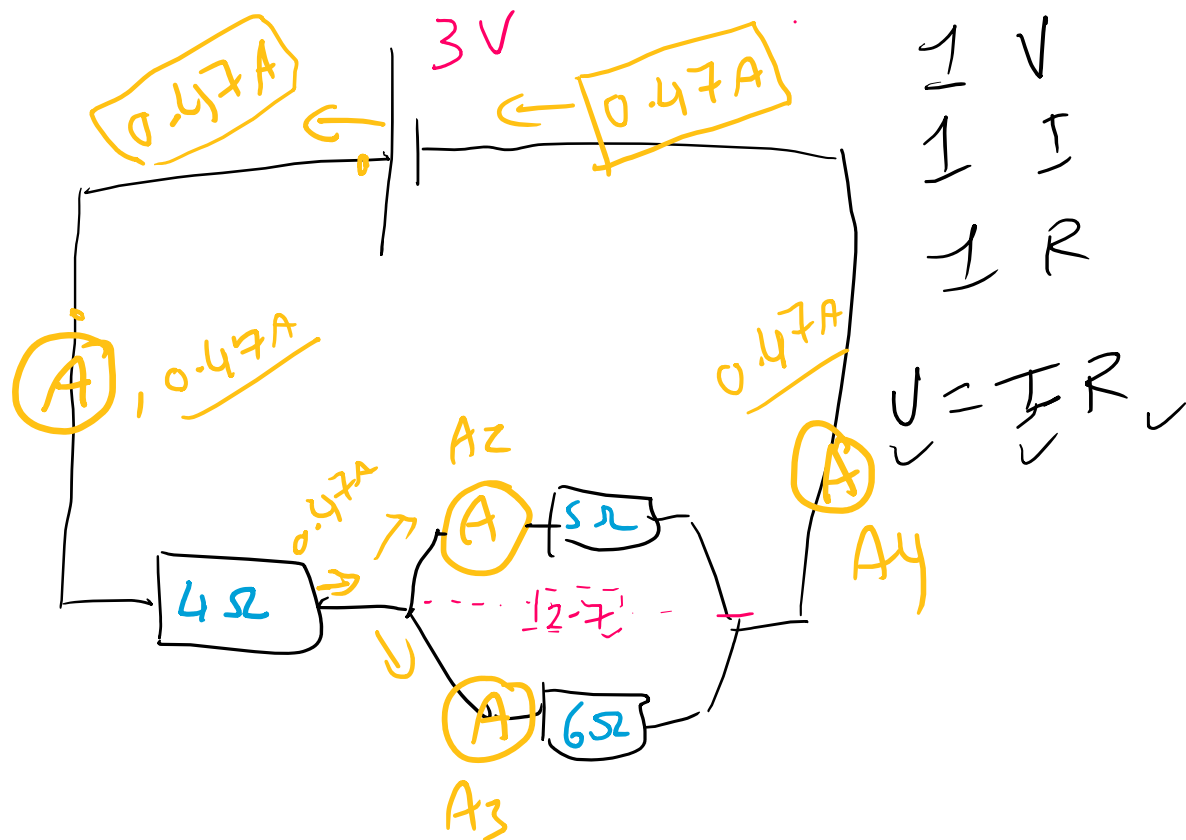
$$I = \frac{V}{R} = \frac{3}{8} = \boxed{0.375 \text{ A}}$$




Current out of the battery is based on the TOTAL resistance of the circuit AND is the same as current returning to the battery.

$$R_{\text{parallel}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 6}{5 + 6} = \frac{30}{11} = \boxed{2.7 \Omega}$$

$$R_{\text{series}} = 4 + 2.7 = \boxed{6.7 \Omega}$$
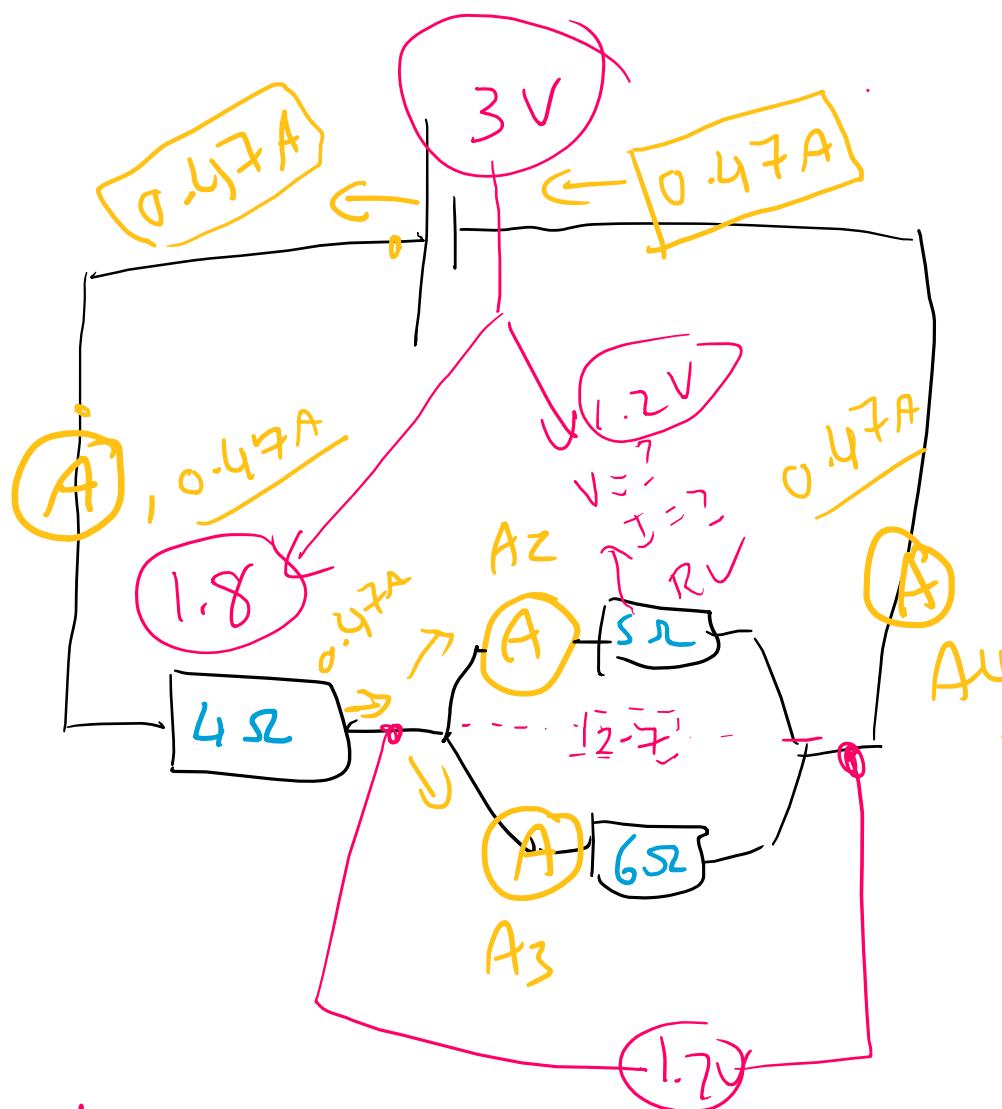
$$I = \frac{V}{R_t} = \frac{3}{6.7} = \boxed{0.47 \text{ A}}$$




$$V_{2.7} = I_{2.7} \times R_{2.7}$$

$$= 0.47 \times 2.7 = \boxed{1.2 \text{ V}}$$

$$V_4 = I_4 \times R_4$$

$$= 0.47 \times 4 = \boxed{1.88 \text{ V}}$$

$$= 3.08 \text{ V}$$

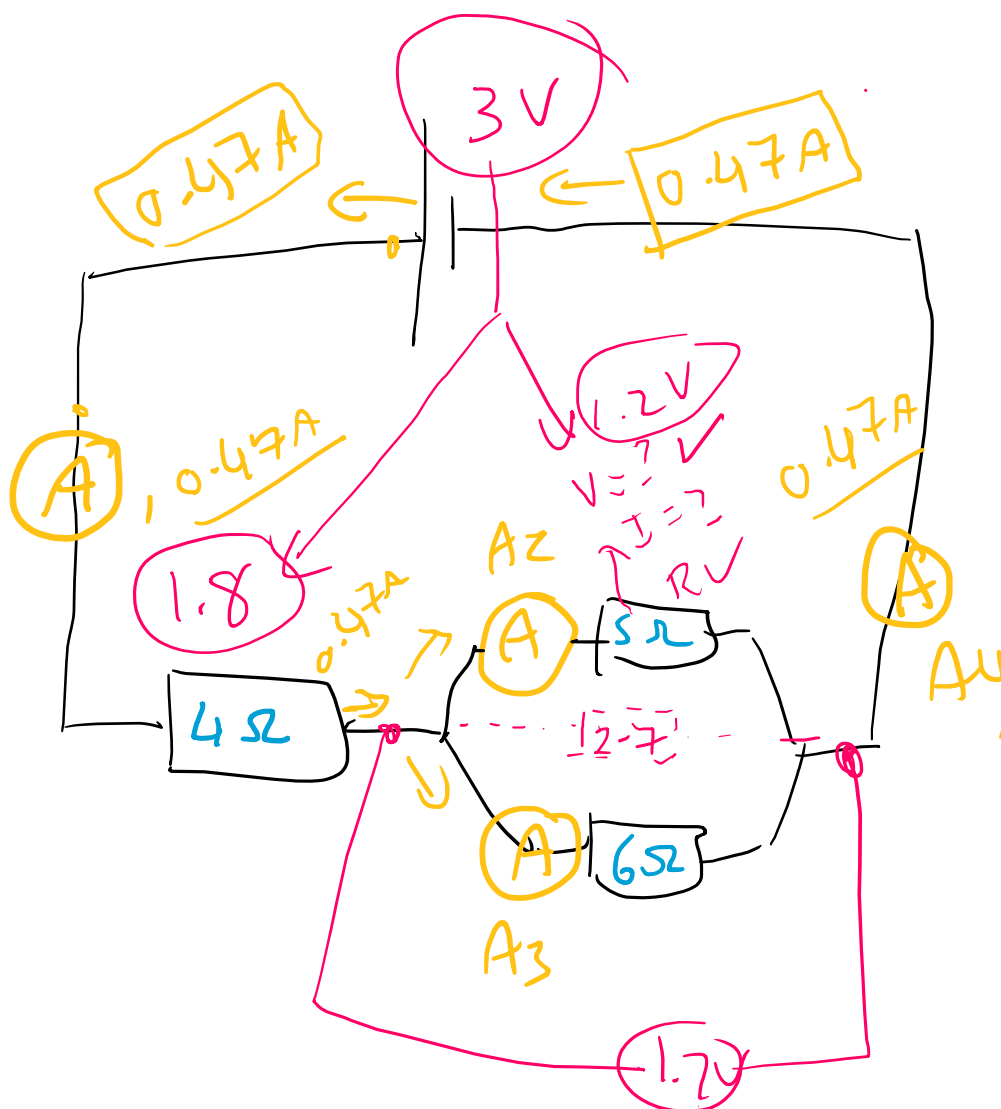

$$V_5 = I_5 R_5$$

$$I = \frac{V}{R} = \frac{1.2}{5} = 0.24A$$


$$V_6 = I_6 R_6$$

$$I = \frac{V}{R} = \frac{1.2}{6} = 0.2A$$

$$I = \boxed{0.44A}$$

Rules

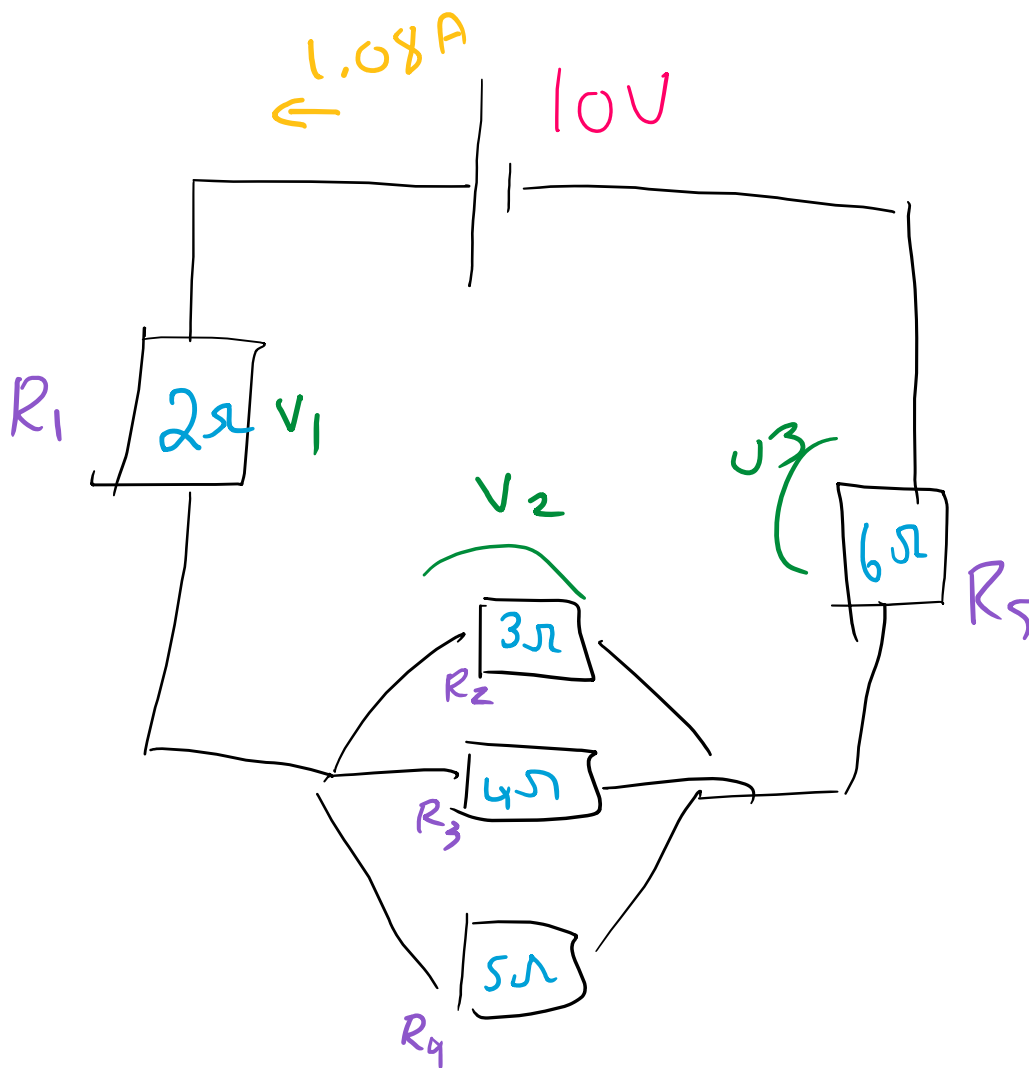- ① Resolve All parallel R 's into equivalent R 's
- ② Resolve All R_s & eq R_s in series
- ③ Get total current of circuit
- ④ Get small V 's
- ⑤ Get small I 's



Step 1

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{4} + \frac{1}{5} = 0.783$$

$$R = \frac{1}{0.783} = 1.276 \Omega$$

Step 2

$$\begin{aligned} R_t &= 2 + 1.276 + 6 \\ &= 9.276 \Omega \end{aligned}$$

Step 3

$$I = \frac{V}{R} = \frac{10}{9.276} = \boxed{1.08 \text{ A}}$$

Step 4

$$V_1 = I R_1 = 1.08 \times 2 = \boxed{2.156 \text{ V}}$$

$$V_2 = I R_{234} = 1.08 \times 1.276 = \boxed{1.38 \text{ V}}$$

$$V_3 = \text{Emf} - V_1 - V_2 = 10 - 2.156 - 1.38 = \boxed{6.47 \text{ V}}$$


or

$$V_3 = I R_5 = 1.08 \times 6 = \boxed{6.48 \text{ V}}$$

Step 5

$$V = I R$$

$$I = \frac{V}{R}$$

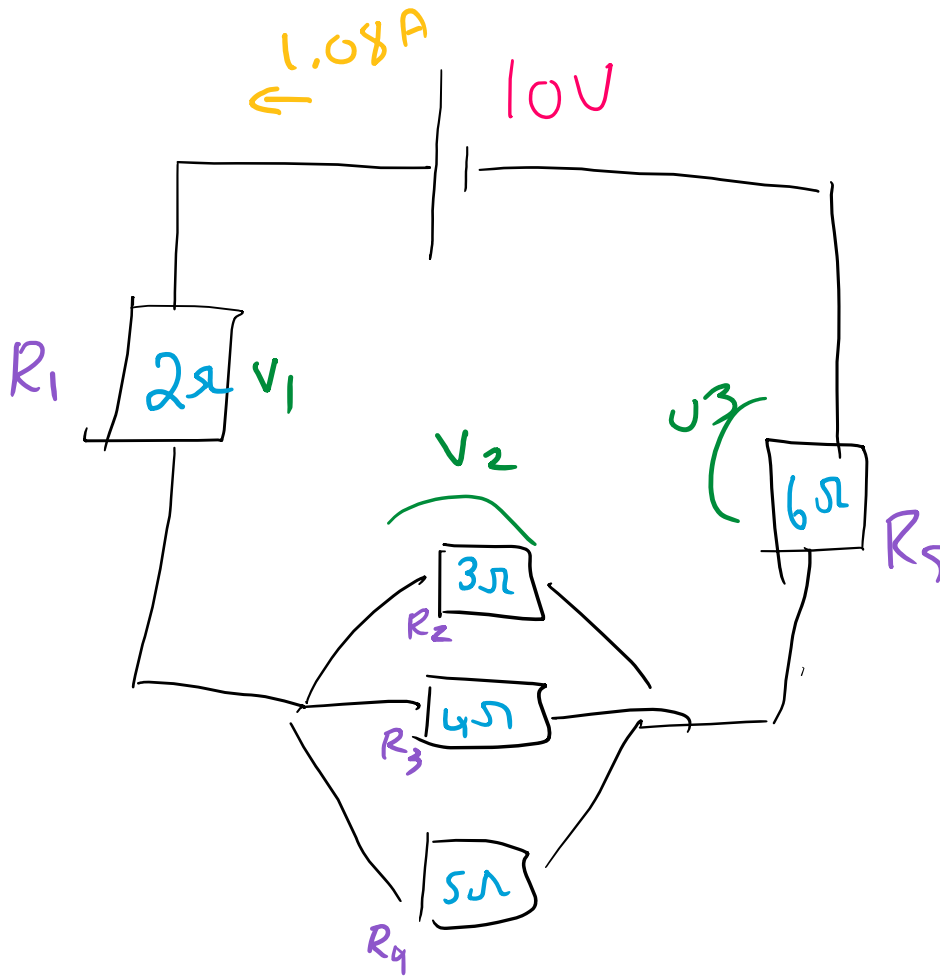

$$I_1 = 1.08 \text{ A}$$

$$I_5 = 1.08 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{1.38}{3} = 0.46 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{1.38}{4} = 0.345 \text{ A}$$

$$I_4 = \frac{V}{R_4} = \frac{1.38}{5} = 0.276 \text{ A}$$

1.08 A